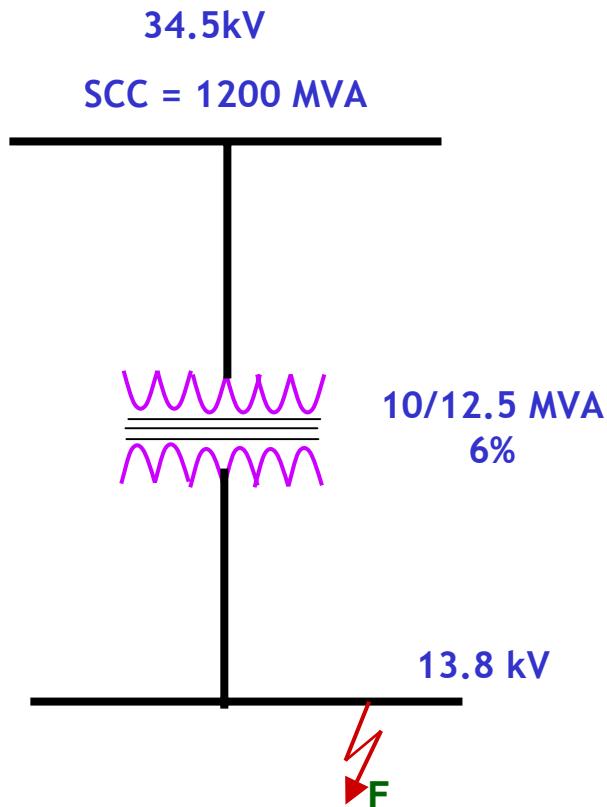

Symmetrical Fault Calculations


Example 1



Calculate the fault current at F

Example 1

Step 1: Calculate Base Values

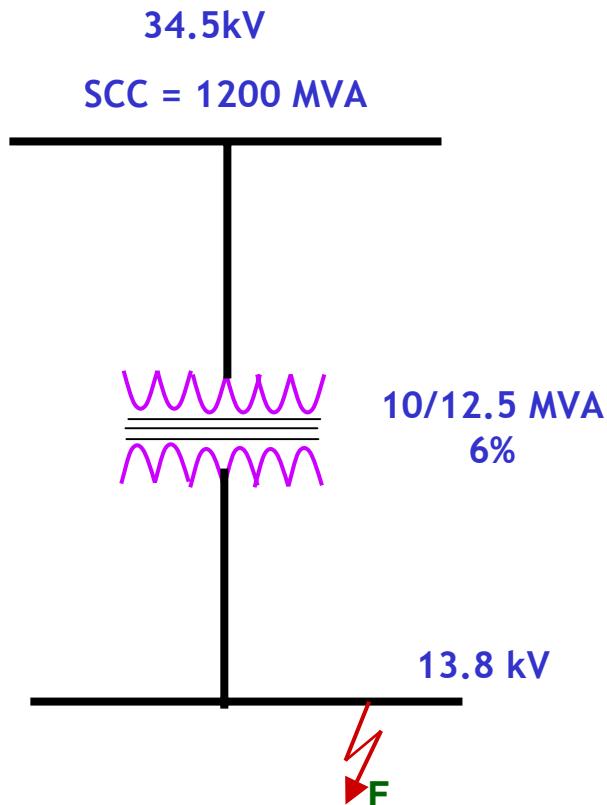

$$MVA_{base} = 100$$

$$kV_{base} = 34.5$$


$$Z_{base} = \frac{kV_{base}^2}{MVA_{base}}$$

$$= \frac{34.5^2}{100} = 11.9 \text{ ohms}$$

$$I_{base} = \frac{MVA_{base}}{kV_{base}} = \frac{100 \text{ MVA}}{34.5 \text{ kV}}$$
$$= 2898.55 \text{ A}$$

Calculate the fault current at F

Example 1

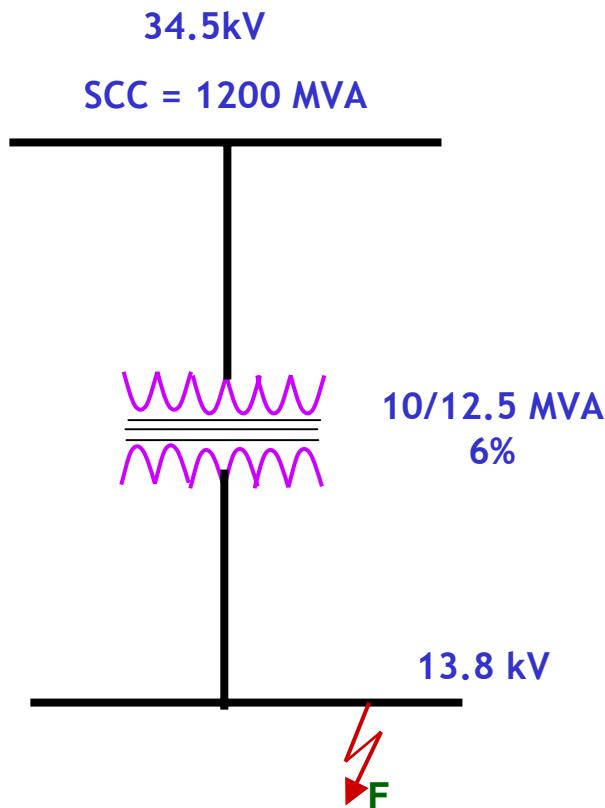


Step 2: Calculate p.u impedances

$$Z_{Tpu} = Z_t \times \frac{MVA_{base}}{MVA_{oldbase}}$$
$$= 0.06 \times \frac{100}{12.5} = 0.48$$

Calculate the fault current at F

Example 1

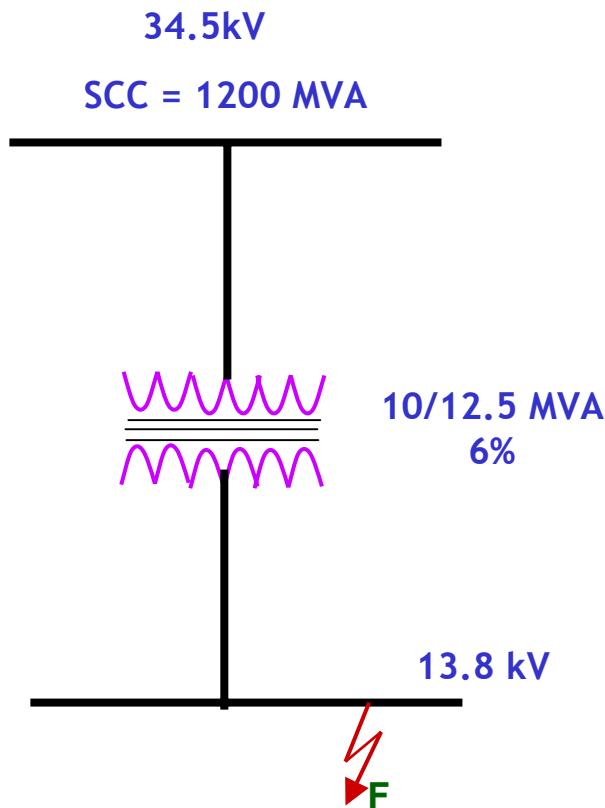


Step 2: Calculate p.u impedances

$$Z_{Tpu} = Z_t \times \frac{MVA_{base}}{MVA_{oldbase}}$$
$$= 0.06 \times \frac{100}{12.5} = 0.48$$

$$Z_{utility} = \frac{MVA_{base}}{MVA_{oldbase}} \times \frac{kV_{oldbase}}{kV_{base}}$$
$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$
$$= 0.0833$$

Calculate the fault current at F

Example 1

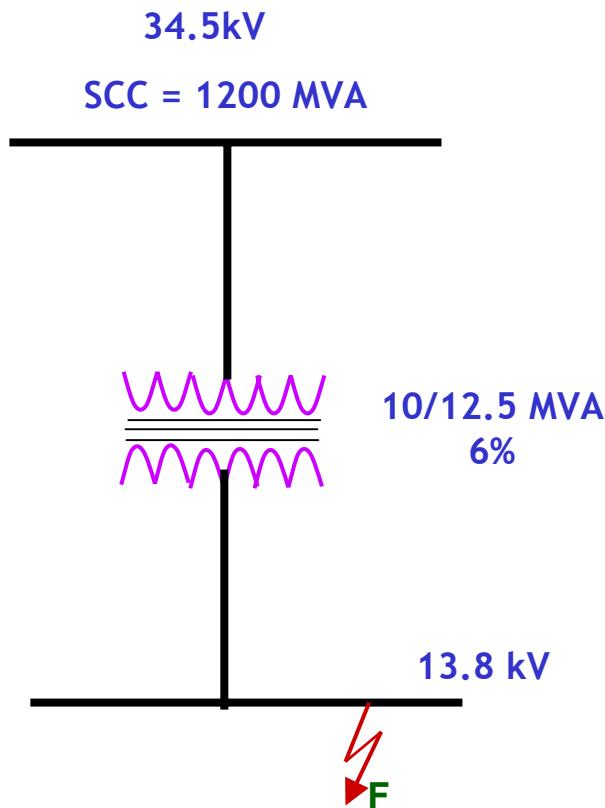


Step 3: Calculate fault current

$$I_{Fpu} = \frac{V_{pu}}{Z_{total}}$$
$$= \frac{1.0}{0.48 + 0.0833} = 1.775 \text{ pu}$$

Calculate the fault current at F

Example 1

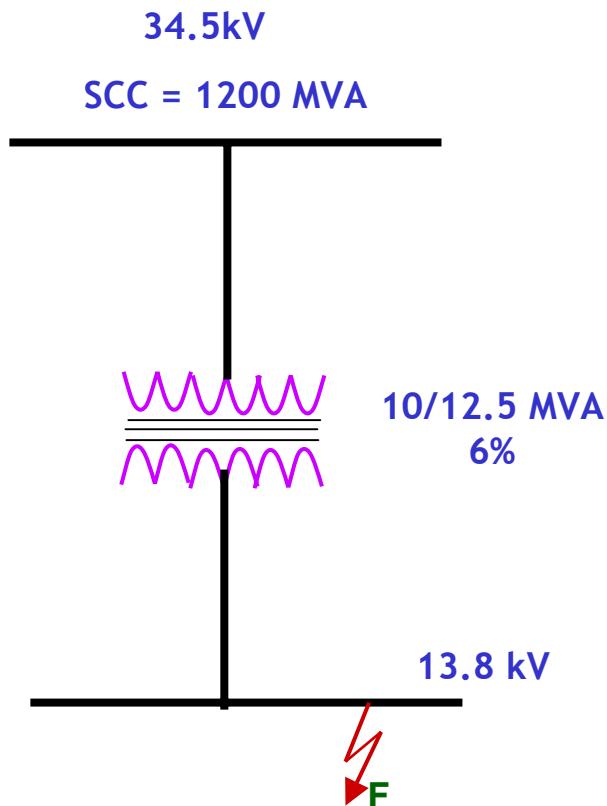

Step 3: Calculate fault current


$$I_{Fpu} = \frac{V_{pu}}{Z_{total}}$$
$$= \frac{1.0}{0.48 + 0.0833} = 1.775 \text{ pu}$$

$$I_{FHV} = I_{Fpu} \times \frac{I_{base}}{\sqrt{3}}$$
$$= 1.775 \times \frac{2898.55}{\sqrt{3}} = 2970 \text{ A}$$

$$I_{FLV} = \frac{I_{FHV}}{13.8} \times 34.5$$
$$= 7426 \text{ A}$$

Calculate the fault current at F


Example 2 - Addition of a Generator

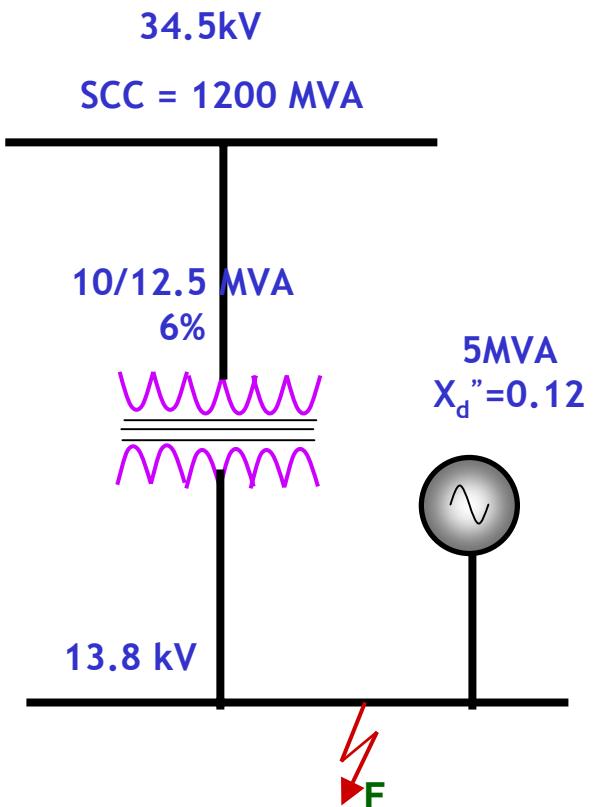

Calculate the fault current at F

Example 2 - Addition of a Generator

Step 1: Calculate impedances

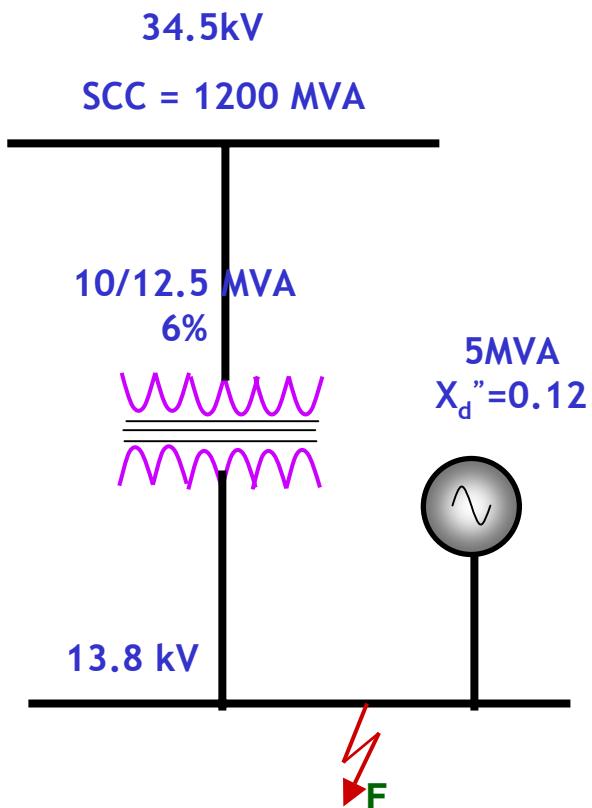


$$Z_{\text{utility}} = \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \times \frac{\text{kV}_{\text{oldbase}}}{\text{kV}_{\text{base}}}$$
$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$
$$= 0.0833$$

Calculate the fault current at F

Example 2 - Addition of a Generator

Step 1: Calculate impedances

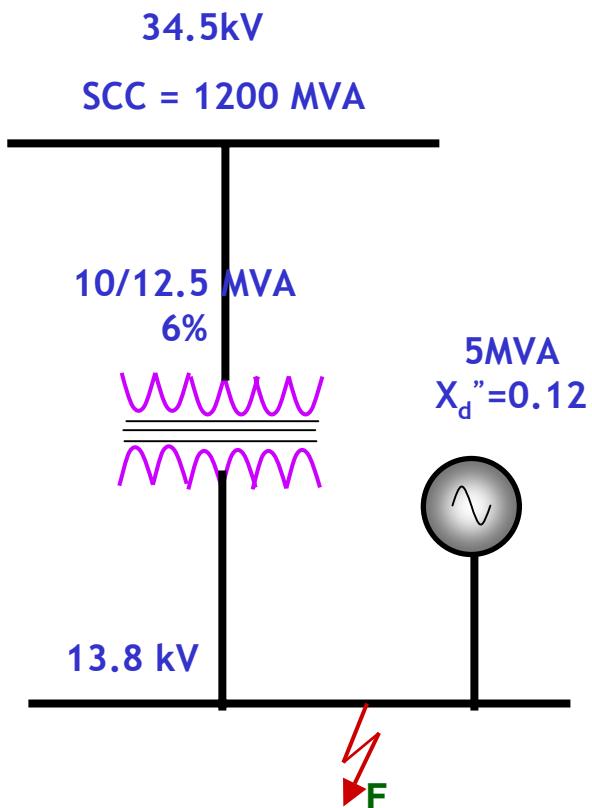


$$Z_{\text{utility}} = \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \times \frac{\text{kV}_{\text{oldbase}}}{\text{kV}_{\text{base}}}$$
$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$
$$= 0.0833$$

$$Z_{\text{Tpu}} = Z_t \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$
$$= 0.06 \times \frac{100}{12.5} = 0.48$$

Calculate the fault current at F

Example 2 - Addition of a Generator

Step 1: Calculate impedances

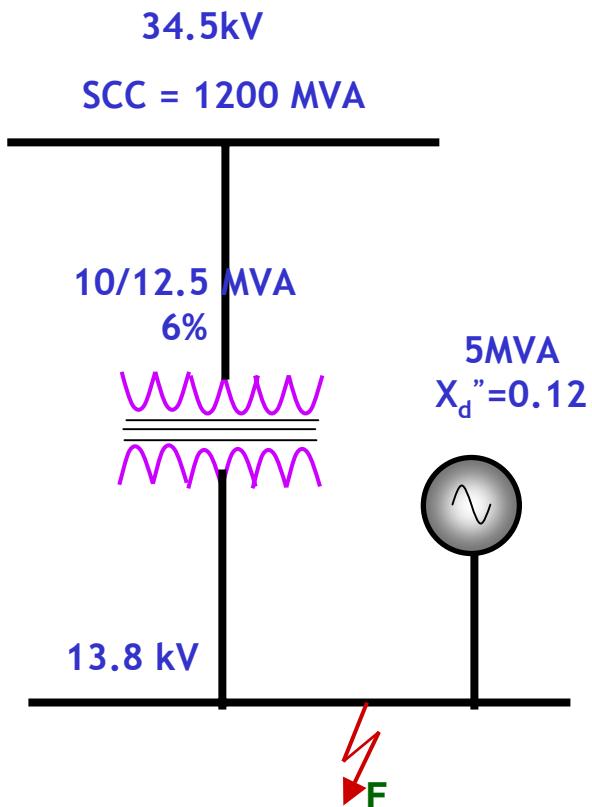

Calculate the fault current at F



$$Z_{\text{utility}} = \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \times \frac{\text{kV}_{\text{oldbase}}}{\text{kV}_{\text{base}}}$$
$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$
$$= 0.0833$$

$$Z_{\text{Tpu}} = Z_t \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$
$$= 0.06 \times \frac{100}{12.5} = 0.48$$

$$Z_{\text{Gpu}} = Z_G \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$
$$= 0.12 \times \frac{100}{5} = 2.4$$

Example 2 - Addition of a Generator


Step 2: Calculate equivalent impedances

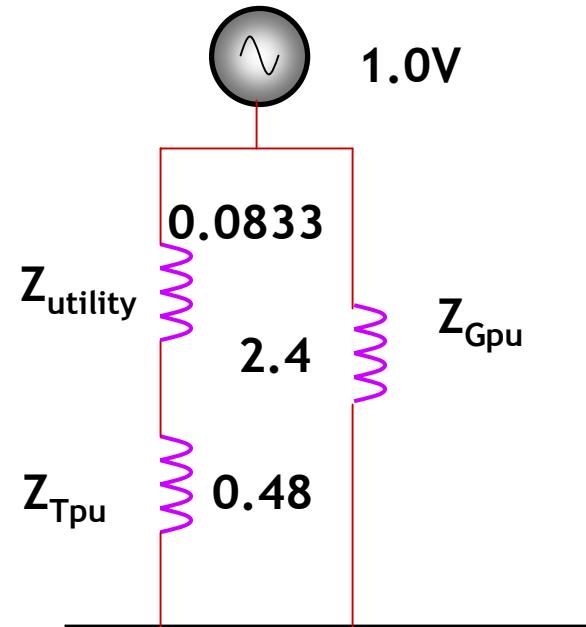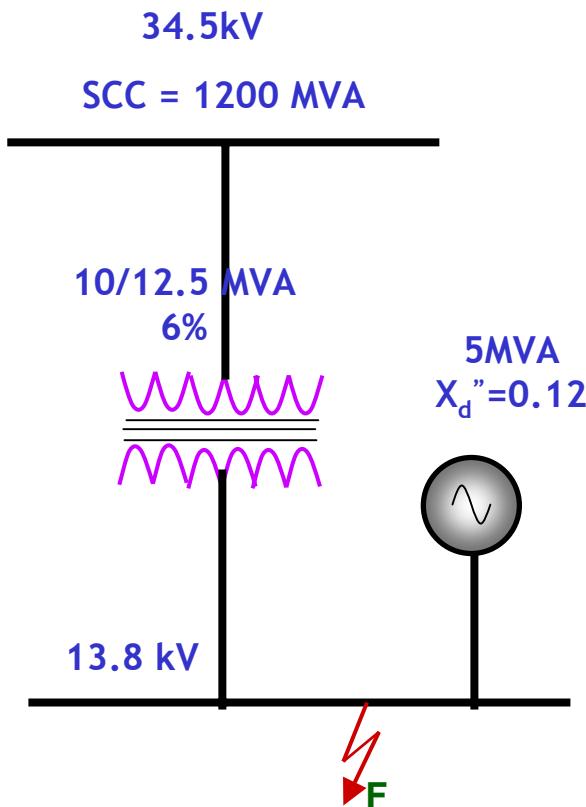

Calculate the fault current at F


Example 2 - Addition of a Generator

Step 2: Calculate equivalent impedances

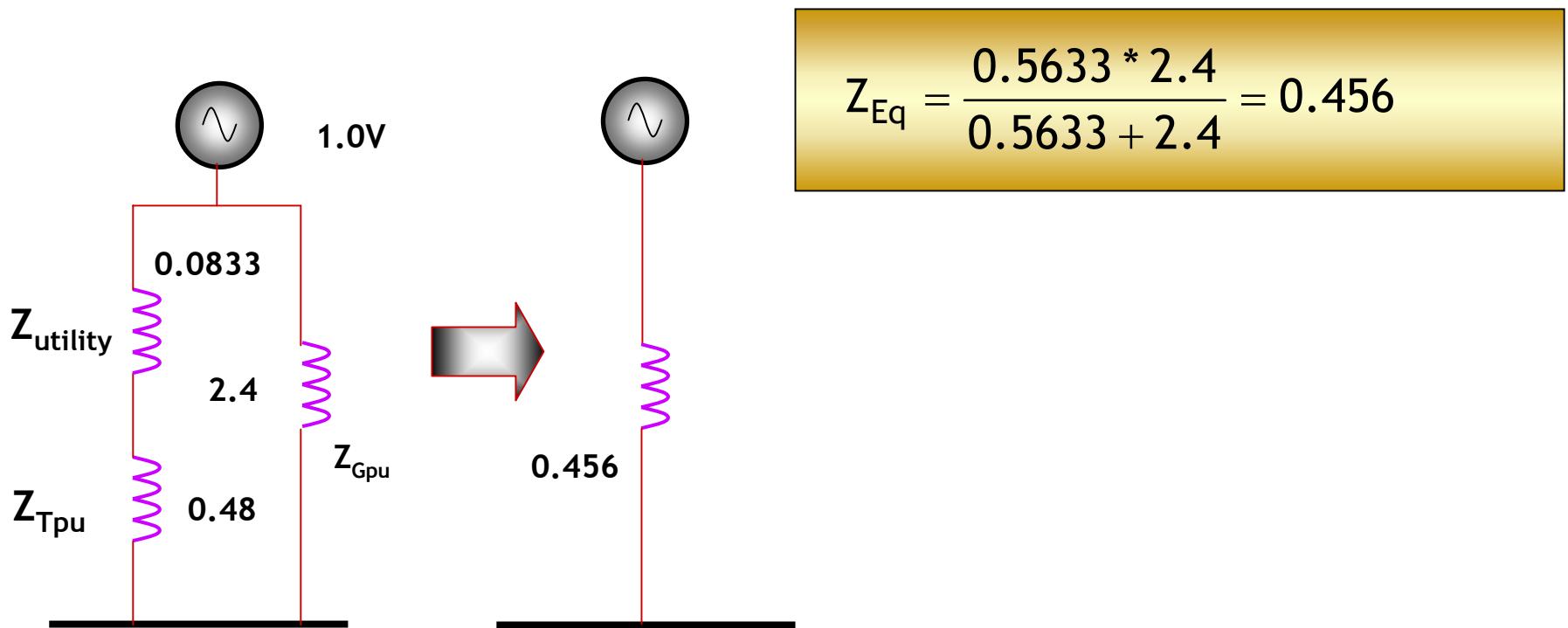

Example 2 - Addition of a Generator

Step 3: Calculate fault current

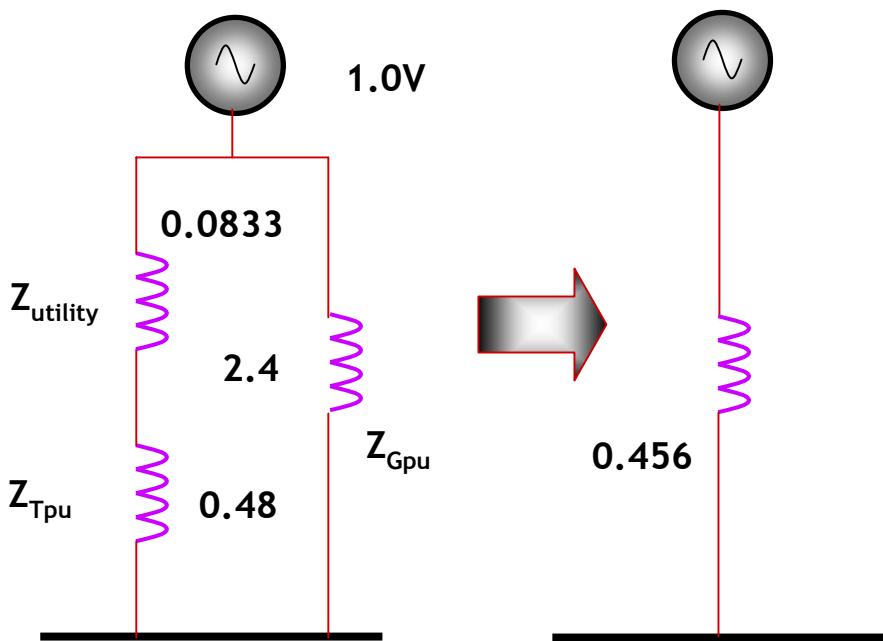


$$Z_{\text{Eq}} = \frac{0.5633 * 2.4}{0.5633 + 2.4} = 0.456$$

$$I_{F\text{pu}} = \frac{V_{\text{pu}}}{Z_{\text{Eq}}} = \frac{1.0}{0.456} = 2.192 \text{ pu}$$

Example 2 - Addition of a Generator

Step 3: Calculate fault current

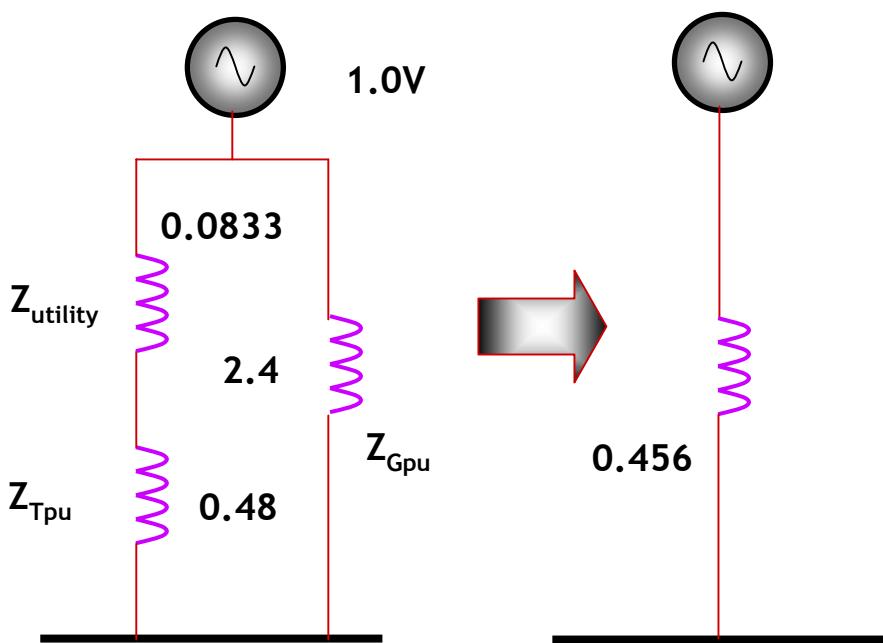


$$Z_{Eq} = \frac{0.5633 * 2.4}{0.5633 + 2.4} = 0.456$$

$$I_{Fpu} = \frac{V_{pu}}{Z_{Eq}} = \frac{1.0}{0.456} = 2.192 \text{ pu}$$


$$\begin{aligned} I_{FHV} &= I_{Fpu} \times \frac{I_{base}}{\sqrt{3}} \\ &= 2.192 \times \frac{2898.55}{\sqrt{3}} = 3668 \text{ A} \end{aligned}$$

$$\begin{aligned} I_{FLV} &= \frac{I_{FHV}}{13.8} \times 34.5 \\ &= 9170 \text{ A} \end{aligned}$$

Example 1 & 2 Comparison

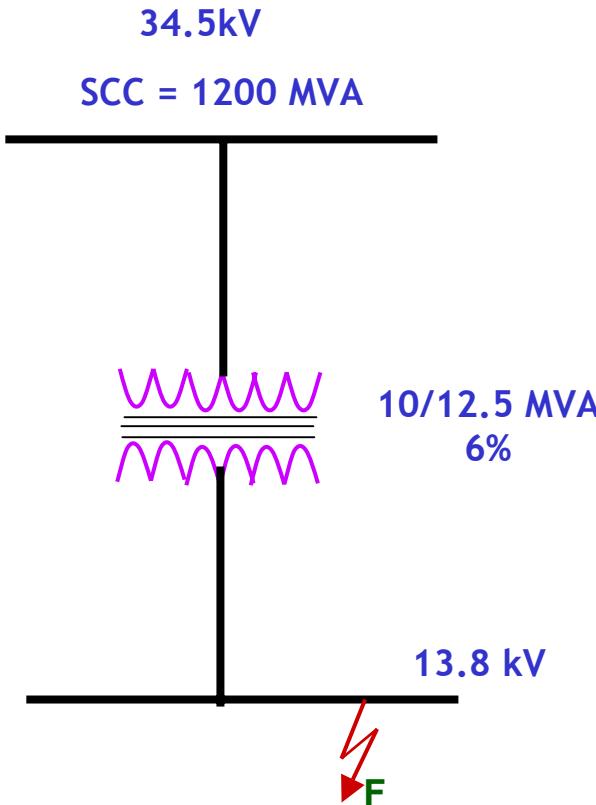


$$I_F = 7426 \text{ Amps}$$

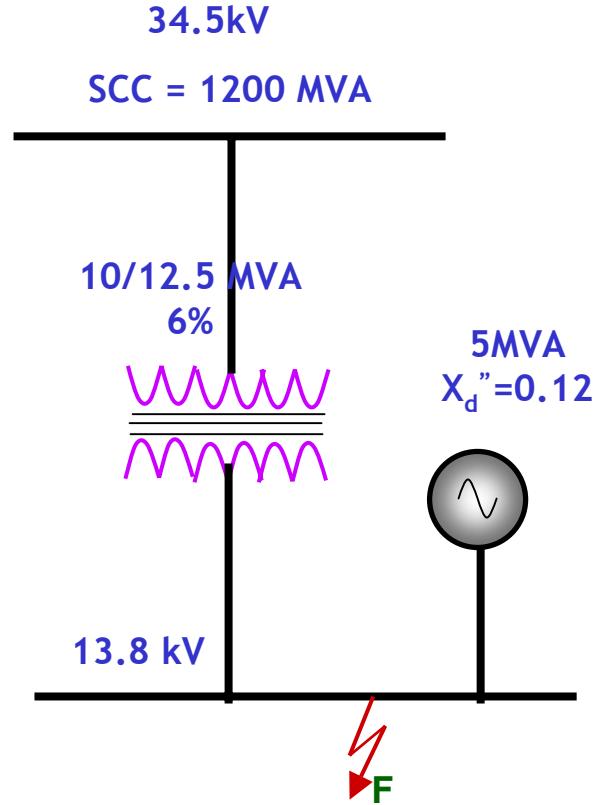

$$I_F = 9170 \text{ Amps}$$

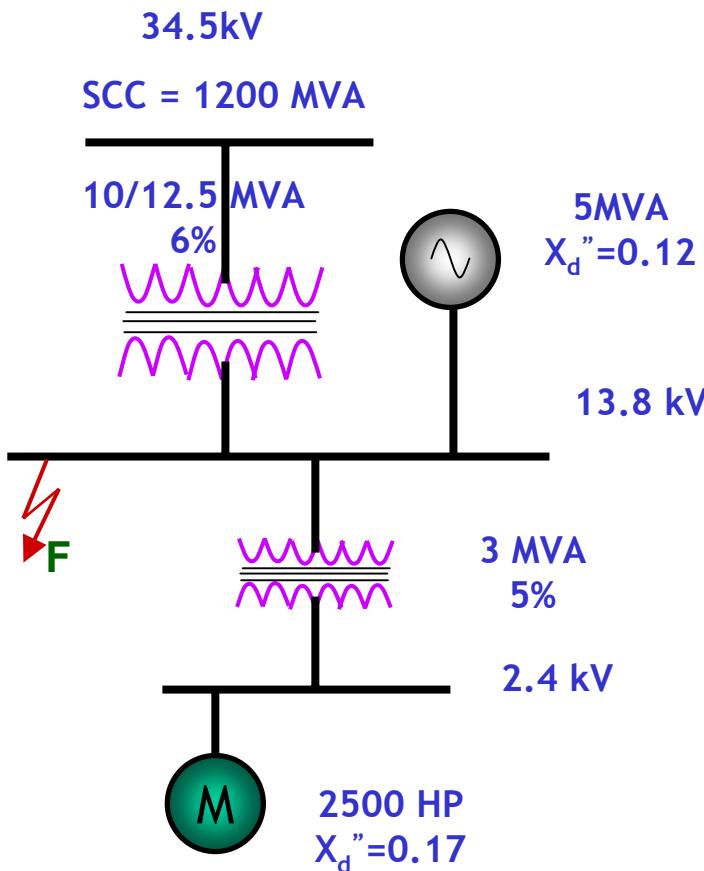
Example 3 -Presence of transformer & motor



Calculate the fault current at F

Example 3 -Presence of transformer & motor

Step 1: Calculate impedances

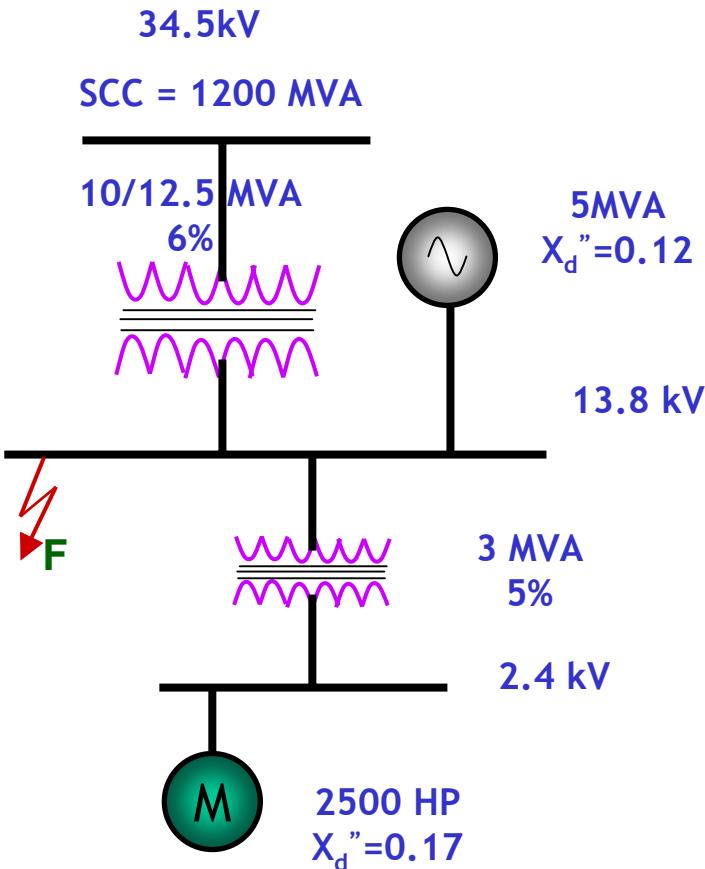


$$Z_{\text{utility}} = \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \times \frac{\text{kV}_{\text{oldbase}}}{\text{kV}_{\text{base}}}$$
$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$
$$= 0.0833$$

Calculate the fault current at F

Example 3 -Presence of transformer & motor

Step 1: Calculate impedances

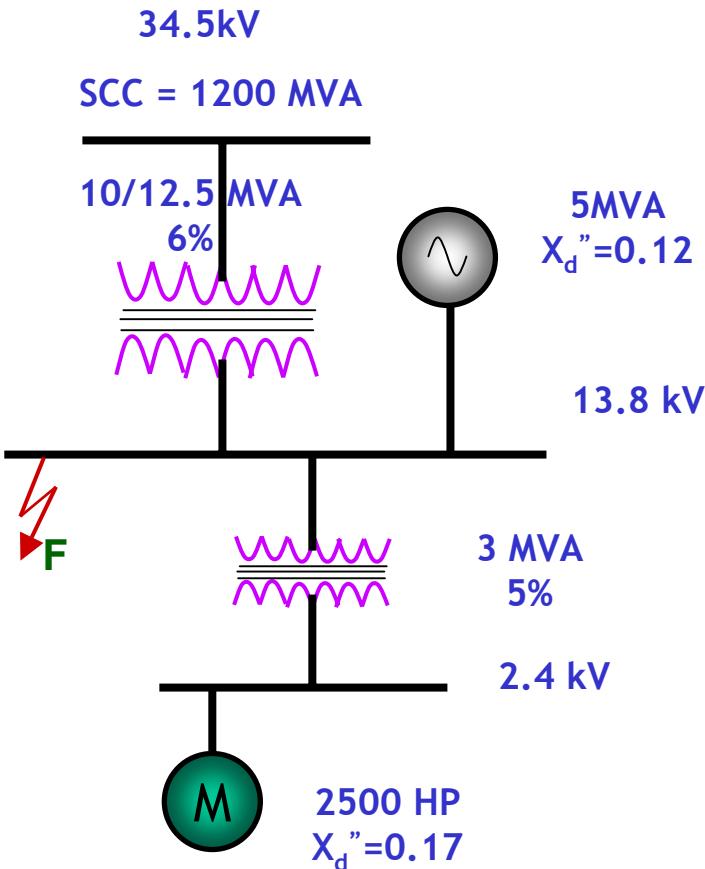


$$Z_{\text{utility}} = \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \times \frac{\text{kV}_{\text{oldbase}}}{\text{kV}_{\text{base}}}$$
$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$
$$= 0.0833$$

$$Z_{Tpu1} = Z_t \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$
$$= 0.06 \times \frac{100}{12.5} = 0.48$$

Calculate the fault current at F

Example 3 -Presence of transformer & motor

Step 1: Calculate impedances

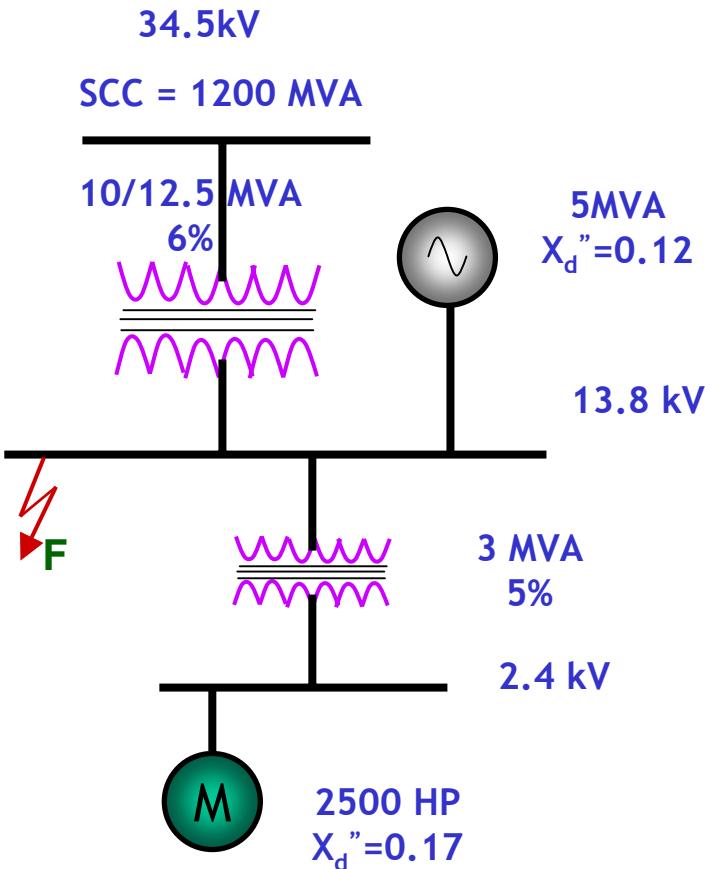

$$Z_{\text{utility}} = \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \times \frac{\text{kV}_{\text{oldbase}}}{\text{kV}_{\text{base}}}$$

$$= \frac{100}{1200} \times \frac{34.5}{34.5}$$

$$= 0.0833$$

$$Z_{Tpu1} = Z_t \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$

$$= 0.06 \times \frac{100}{12.5} = 0.48$$


$$Z_{Gpu} = Z_G \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$

$$= 0.12 \times \frac{100}{5} = 2.4$$

Calculate the fault current at F

Example 3 -Presence of transformer & motor

Step 1: Calculate impedances

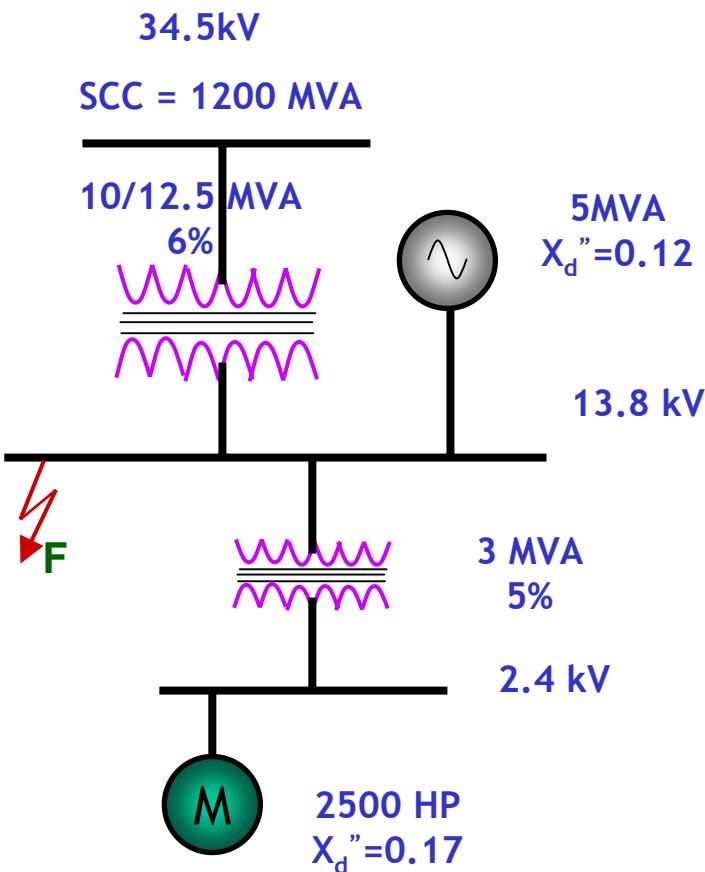

$$Z_{\text{utility}} = 0.0833 \text{ pu}$$

$$Z_{T\text{pu}1} = 0.48 \text{ pu}$$


$$Z_{G\text{pu}} = 2.4 \text{ pu}$$

$$\begin{aligned} Z_{T\text{pu}2} &= Z_t \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}} \\ &= 0.05 \times \frac{100}{3} = 1.667 \end{aligned}$$

Calculate the fault current at F

Example 3 -Presence of transformer & motor

Step 1: Calculate impedances

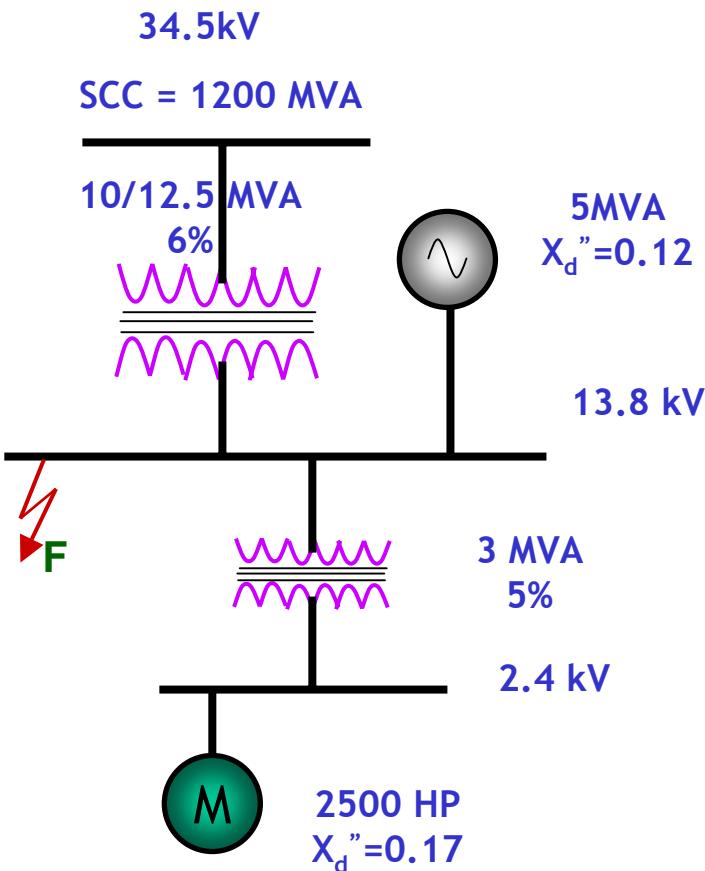

$$Z_{\text{utility}} = 0.0833 \text{ pu}$$

$$Z_{T\text{pu}1} = 0.48 \text{ pu}$$

$$Z_{G\text{pu}} = 2.4 \text{ pu}$$

$$Z_{T\text{pu}2} = 1.667 \text{ pu}$$

$$\text{Motor rating} = \frac{2500 * 0.746}{\text{pf}}$$

$$= \frac{1865}{0.866} = 2154$$


$$Z_{M\text{pu}} = Z_m \times \frac{\text{MVA}_{\text{base}}}{\text{MVA}_{\text{oldbase}}}$$

$$= 0.17 \times \frac{100}{2.154} = 7.89$$

Calculate the fault current at F

Example 3 -Presence of transformer & motor

Step 1: Calculate impedances

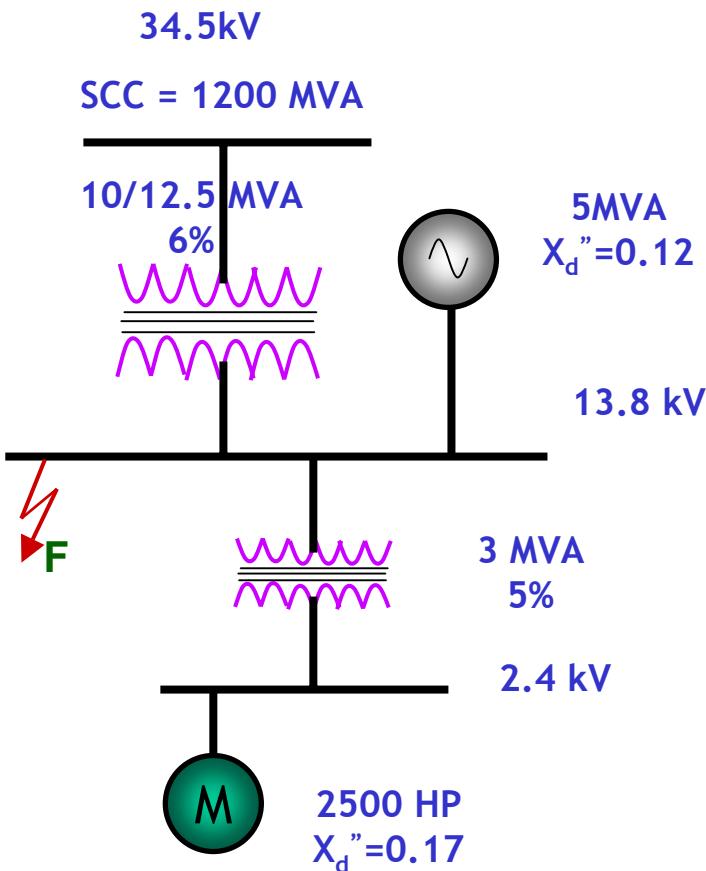

$$Z_{\text{utility}} = 0.0833 \text{ pu}$$

$$Z_{T\text{pu}1} = 0.48 \text{ pu}$$

$$Z_{G\text{pu}} = 2.4 \text{ pu}$$



$$Z_{T\text{pu}2} = 1.667 \text{ pu}$$

$$Z_{M\text{pu}} = 7.89 \text{ pu}$$

Calculate the fault current at F

Example 3 -Presence of transformer & motor


Step 2: Calculate Equivalent impedances

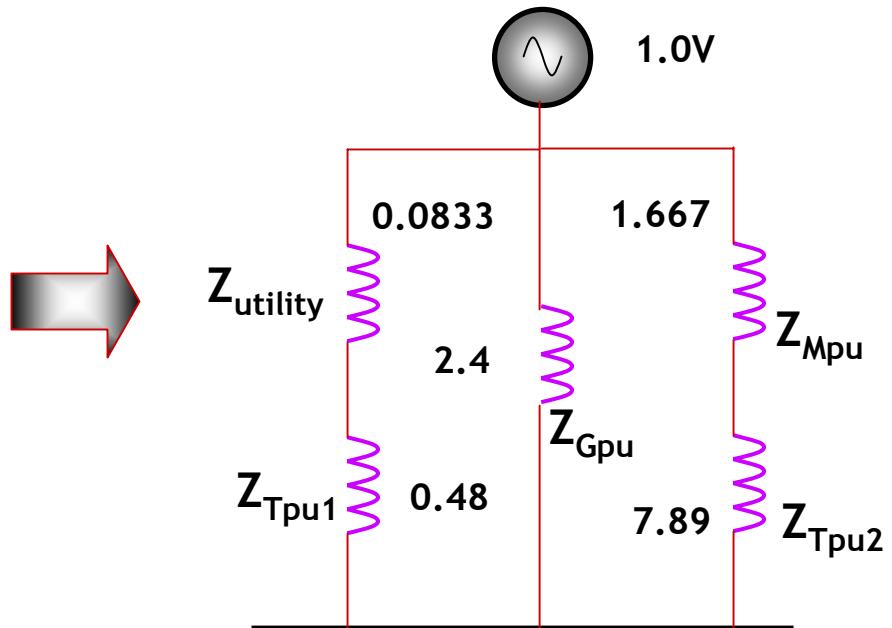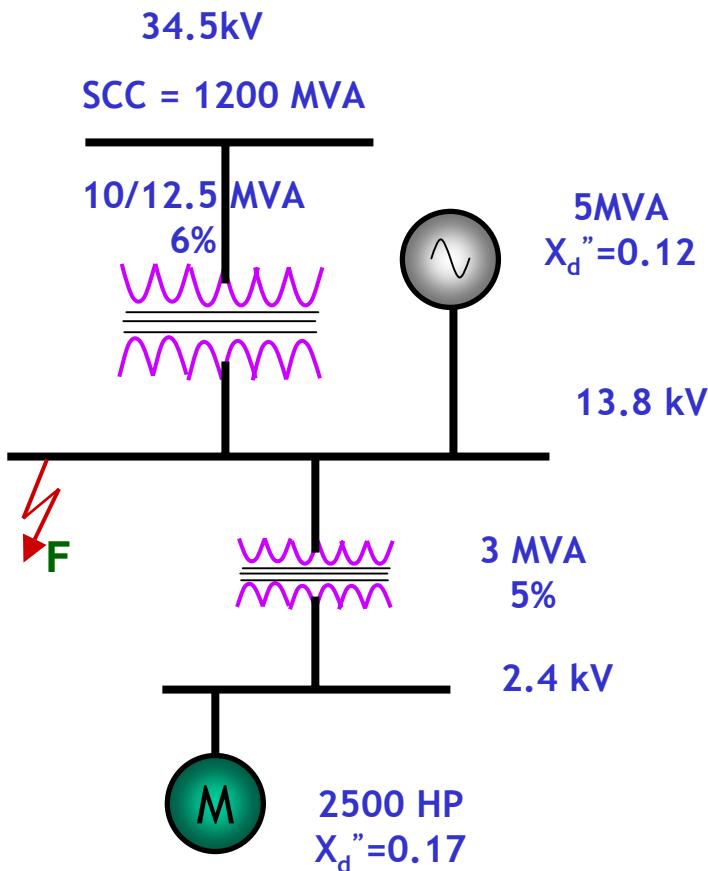

Calculate the fault current at F


Example 3 -Presence of transformer & motor

Step 2: Calculate Equivalent impedances

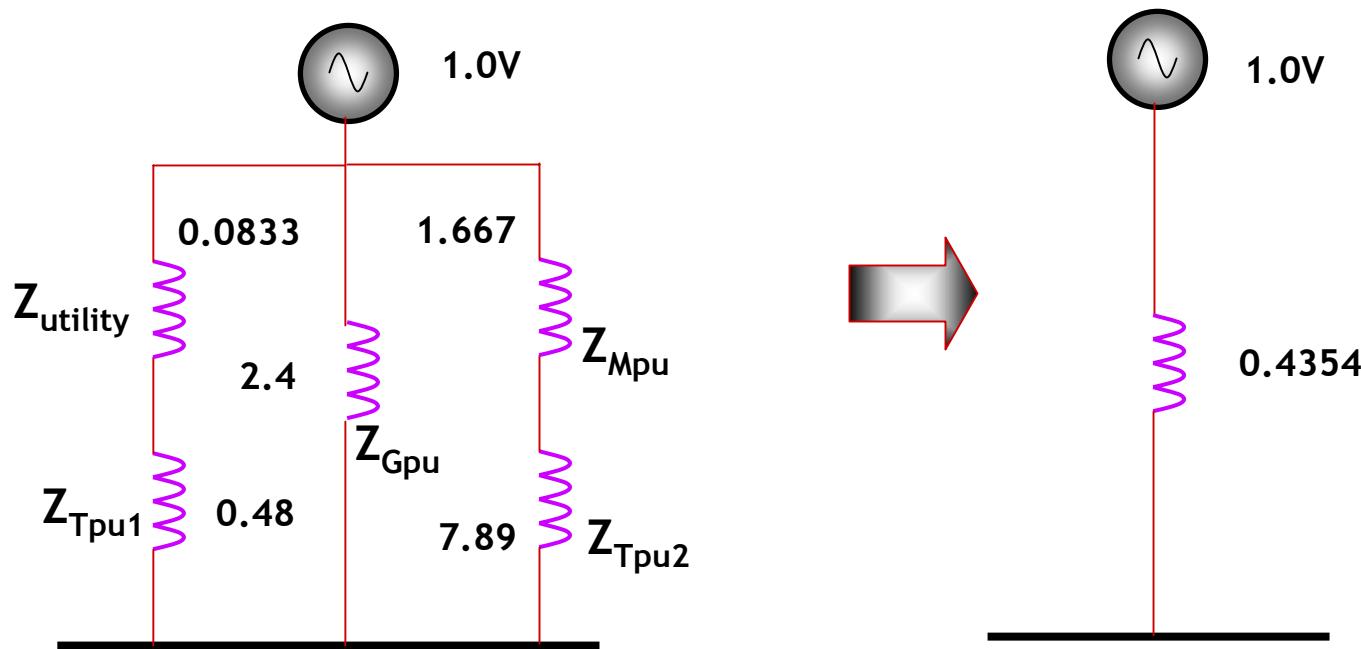

Example 3 -Presence of transformer & motor

Step 3: Calculate fault current

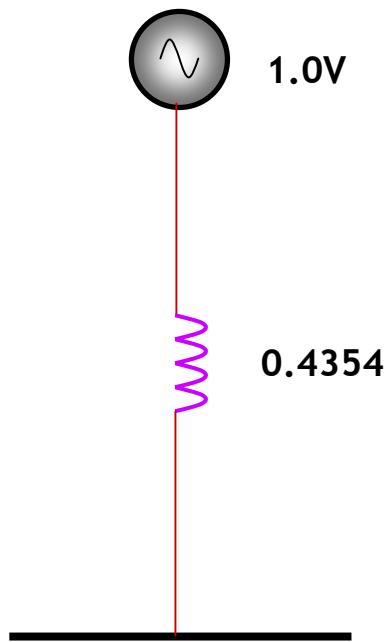

$$I_{Fpu} = \frac{V_{pu}}{Z_{Eq}} = \frac{1.0}{0.4354} = 2.297 \text{ pu}$$

$$I_{FHV} = I_{Fpu} \times \frac{I_{base}}{\sqrt{3}}$$
$$= 2.297 \times \frac{2898.55}{\sqrt{3}} = 3844 \text{ A}$$

$$I_{FLV} = \frac{I_{FHV}}{13.8} \times 34.5$$
$$= 9609 \text{ A}$$

Symmetrical Fault

